

MSC8122 and MSC8126 Power Circuit Design Recommendations and Examples

by Moty Groissman and Boaz Kfir

This application note discusses recommendations for designing power circuits to support correct power-up and power-down sequencing for MSC8122 and MSC8126 devices. The document discusses possible solutions using known board examples.

CONTENTS

1	MSC8122 and MSC8126 Power-Up Sequence ..2
2	On-Board 3.3 V and 1.2 V Power Regulators3
3	Migration of MSC8102 Designs.....3
4	External 3.3 V Supply.....5

1 MSC8122 and MSC8126 Power-Up Sequence

The power-up sequence must follow the guidelines shown in **Figure 1**.

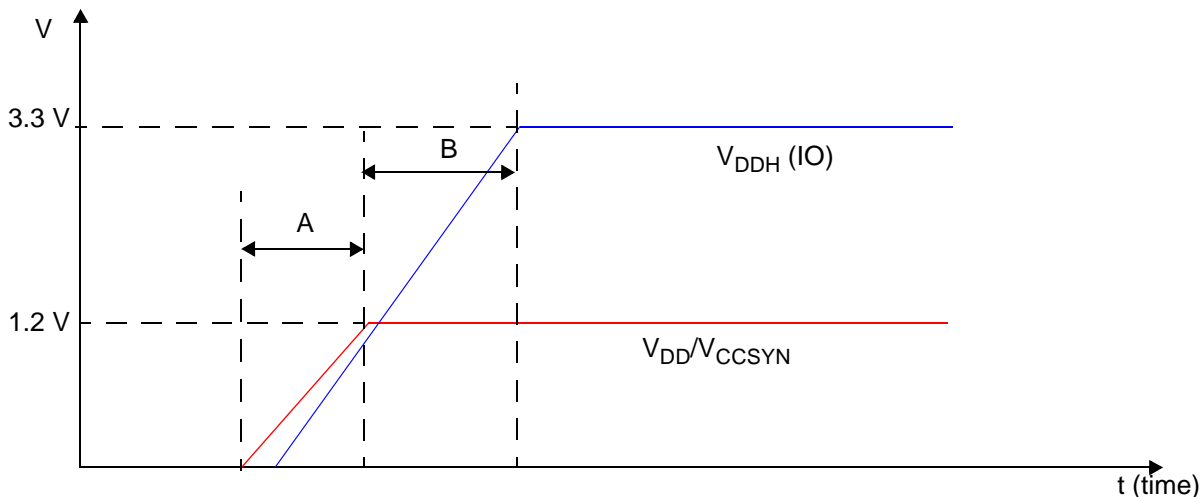


Figure 1. Power-Up Sequence for V_{DDH} and V_{DD}/V_{CCSYN}

The following rules apply:

1. During time interval A, V_{DDH} should always be equal to or less than the V_{DD}/V_{CCSYN} voltage level. The duration of interval A should be kept below 10 ms.
2. The duration of timing interval B should be kept as small as possible and less than 10 ms.

Note: In the following sections, every reference to V_{DD} also applies to V_{CCSYN} .

Note: Make sure that V_{DD} is never greater than 0.8 V higher than V_{DDH} during the power-up sequence. If the $V_{DD} - V_{DDH} > 0.8$ V, current can flow from the VDD supply to the VDDH supply through the ESD protection circuit. Use one of the following two methods to avoid the generation of this current:

- Design the circuits so that V_{DD} can never rise to a level greater than $V_{DDH} + 0.8$ V.
- Add a current limiting resistor (10 Ω minimum) to GND for the V_{DDH} supply. With such a design, when the V_{DDH} supply is off, it has with an initial level of $V_{DD} - 0.8$ V.


See the product data sheet for power supply limits and specifications.

2 On-Board 3.3 V and 1.2 V Power Regulators

The following examples offers two possible on-board power supply designs that can support the recommended power-up sequence.

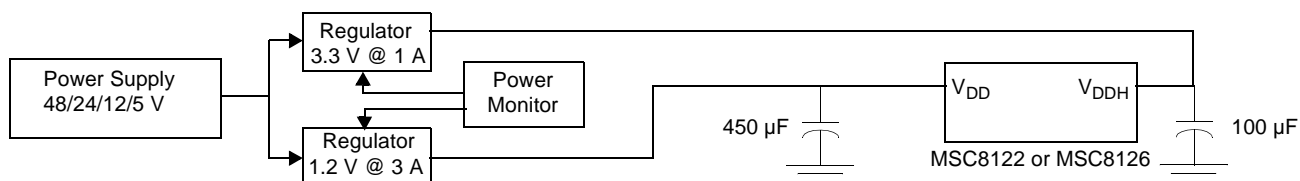2.1 Two Regulators And a Power Monitor Unit

The preferred method of supplying sequenced power from on-board supplies is to use two power regulators operating in parallel and controlled by a power monitor unit as shown in **Figure 1**. The power monitor unit controls the order and timing of the power-up sequence. The advantage of using the power monitor is that you can tune the rise and fall of both supplies without reference to the individual loads on each supply.



Note: The power control unit should prevent V_{DD} from ever being > 0.8 V higher than V_{DDH} .

Figure 2. Two Parallel Regulators with Power Monitor

2.2 Two Regulators with No Power Monitor

You can also use two regulators in parallel without a power monitor unit, as shown in **Figure 3**. You should verify that the design conforms to the recommended power-up/power-down design guidelines independent of the loading of the both regulators. You can also use the suggested solution in **Section 3**.

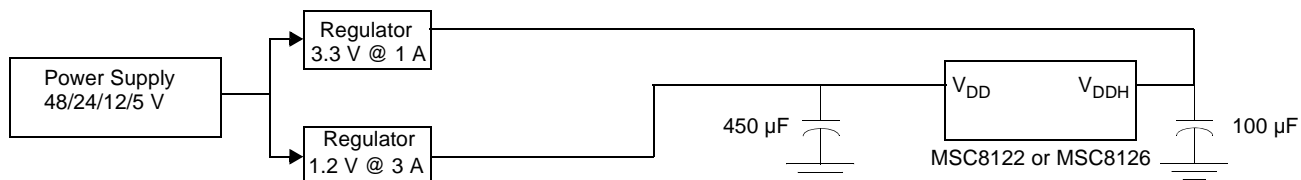


Figure 3. Two Parallel Regulators with No Power Monitor

Note: Make sure that V_{DD} is never greater than 0.8 V higher than V_{DDH} during the power-up sequence.

3 Migration of MSC8102 Designs

This example uses two regulators in parallel with a bias circuit as shown in **Figure 4** similar to the one recommended for MSC8102 designs. In some configurations however, loading conditions can cause the regulator for V_{DDH} to raise the 3.3 V level first, which violates the MSC8122 power-up guidelines. To prevent this, use the

special circuit shown in **Figure 5** between the source power supply, the 3.3 V regulator output, and the 1.2 V regulator output. The design was verified using one MSC8122 device and was shown to maintain the proper power-up sequence for the MSC8122 device.

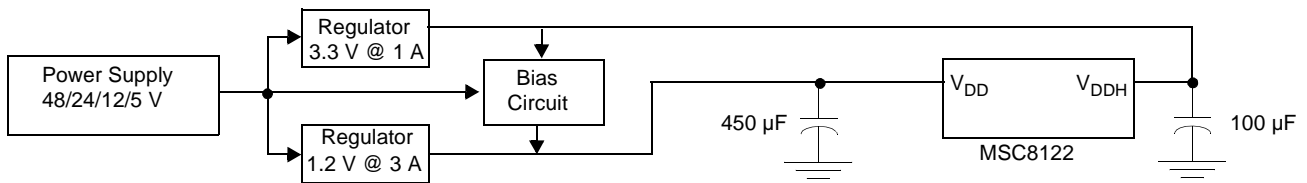


Figure 4. Two Regulators in Parallel With a Bias Circuit

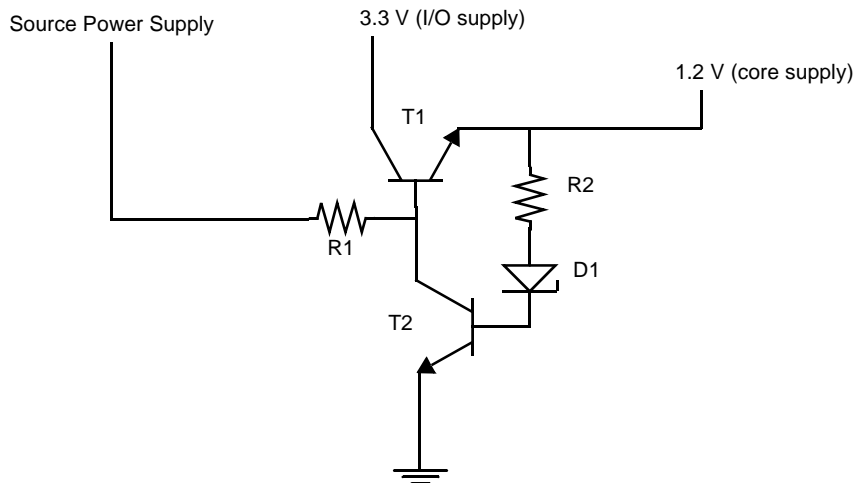


Figure 5. Example Voltage Regulator Circuit

As the supply voltage rises, base current drawn through resistor R1 turns transistor T1 off. Current from the 3.3 V supply moves to the core V_{DD} rail and charges the on-board decoupling capacitors. When the voltage on the core V_{DD} rail rises to ~ 0.8 V, current begins to pass through R2 and D1 to the base of T2. This current switches transistor T2 on, which connects ground to the base of the T1. The resulting ground level on the base of T1 switches off T1. The potential on the core V_{DD} rail falls, and that closes T2 and opens T1. This state continues until the core V_{DD} voltage regulator does not turn on and the voltages become stable.

Note: Make sure that V_{DD} is never greater than 0.8 V higher than V_{DDH} during the power-up sequence.

4 External 3.3 V Supply

V_{DDH} can be generated directly from an external 3.3 V supply, and the circuit can use a single voltage regulator to generate the V_{DD} for the core voltage as shown in **Figure 6**. Because the 3.3 V connects directly to the MSC8122 or MSC8126 device and V_{DD} is generated from the same source, application of the 3.3 V level should be delayed until the V_{DD} supply rises to its nominal level. The 3.3 V supply is controlled by a switch mechanism that does not close until V_{DD} is at the required voltage level. Refer to the technical data sheet for your device for the V_{DD} specifications.

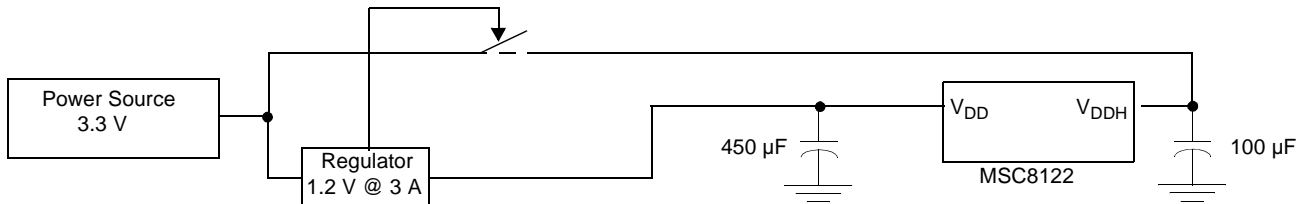


Figure 6. I/O Supply Using a Switching Element

Figure 7 shows a block diagram of this configuration. The reference voltage needs to be checked against the V_{DD} core voltage. The switch should only open when V_{DD} rises to ~ 1.0 V.

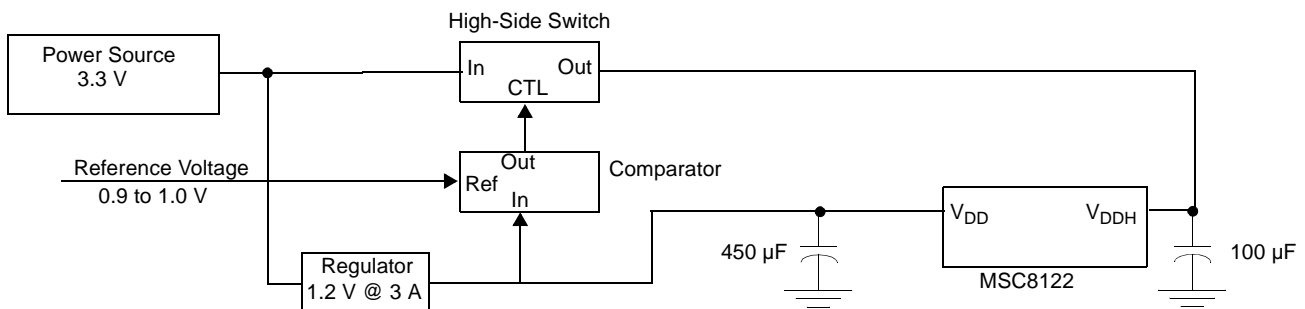


Figure 7. I/O Switching Example Block Diagram

Figure 8 shows the circuit that was verified on a Freescale evaluation board.

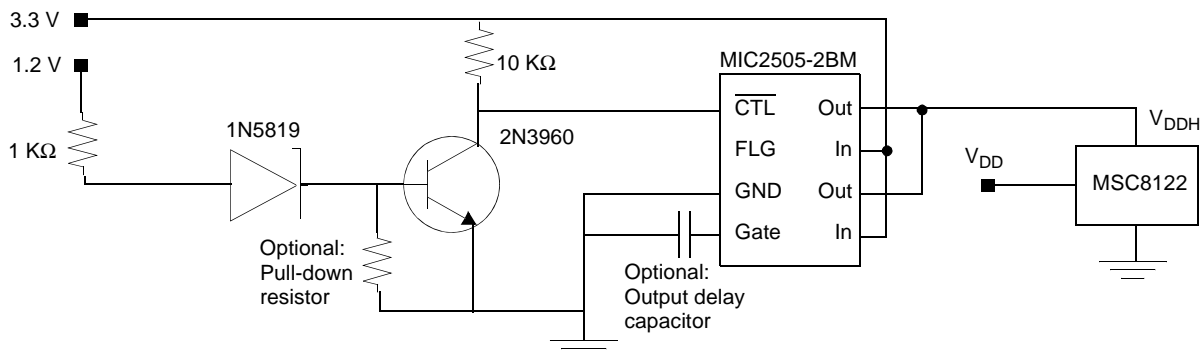


Figure 8. Tested Implementation of V_{DDH} Switch Logic

In this example, the reference voltage is derived from the 1.2 V regulator output. The control of the high-side switch goes low when the 1.2 V regulator output voltage rises to 1.0 V. The MIC2505-2BM switch control (\overline{CTL}) signal is active low.

Because the circuit shown in **Figure 8** delays applying the 3.3 V to the MSC8122 device, there could be a potential problem with logical 1 inputs to the MSC8122 device from other parts on the board. To minimize this problem, we recommend that you use the switched 3.3 V for other system devices as well as the MSC8122 device so that the design supplies the 3.3 V power to all parts simultaneously.

If the design must use the switched 3.3 V power only with the MSC8122 device, you must consider the following:

- Each input that is driven to a 1 state during power-up may draw up to 80 mA. Compute the total possible power draw per input using the following equation:

$$\text{current for one input pin} = (V_{DDH} - 0.7 \text{ V}) / (R_{\text{driver}} + R_{\text{board}} + 7 \Omega) \quad \text{Equation 1}$$

where,

R_{driver} = the resistance of the driver circuit

R_{board} = the resistance of the board

From the equation, it can be seen that any resistor put on board decreases the current draw.

- To minimize current through the inputs, drive all inputs to a logical 0 until the MSC8122 device V_{DDH} reaches its nominal level.
- Any pin that connects to MSC8122 devices on the board and drives a logical 1 causes current that increases according to the number of MSC8122 devices connected. The current draw for multiple MSC8122 devices being driven is:

$$\text{current for shared input pins} = (V_{DDH} - 0.7 \text{ V}) / (R_{\text{driver}} + R_{\text{board}} + 7 \Omega / N) \quad \text{Equation 2}$$

where,

R_{driver} = the resistance of the driver circuit

R_{board} = the resistance of the board

N = the total number of MSC8122 devices driven

- Connect unused input pins to their non-active value (pulled up or pulled down) via resistors.

How to Reach Us:

Home Page:

www.freescale.com

Web Support:

<http://www.freescale.com/support>

USA/Europe or Locations Not Listed:

Freescale Semiconductor, Inc.
 Technical Information Center, EL516
 2100 East Elliot Road
 Tempe, Arizona 85284
 +1-800-521-6274 or
 +1-480-768-2130
www.freescale.com/support

Europe, Middle East, and Africa:

Freescale Halbleiter Deutschland GmbH
 Technical Information Center
 Schatzbogen 7
 81829 Muenchen, Germany
 +44 1296 380 456 (English)
 +46 8 52200080 (English)
 +49 89 92103 559 (German)
 +33 1 69 35 48 48 (French)
www.freescale.com/support

Japan:

Freescale Semiconductor Japan Ltd.
 Headquarters
 ARCO Tower 15F
 1-8-1, Shimo-Meguro, Meguro-ku
 Tokyo 153-0064
 Japan
 0120 191014 or
 +81 3 5437 9125
support.japan@freescale.com

Asia/Pacific:

Freescale Semiconductor Hong Kong Ltd.
 Technical Information Center
 2 Dai King Street
 Tai Po Industrial Estate
 Tai Po, N.T., Hong Kong
 +800 2666 8080
support.asia@freescale.com

For Literature Requests Only:

Freescale Semiconductor
 Literature Distribution Center
 P.O. Box 5405
 Denver, Colorado 80217
 +1-800 441-2447 or
 +1-303-675-2140
 Fax: +1-303-675-2150
LDCForFreescaleSemiconductor@hibbertgroup.com

Information in this document is provided solely to enable system and software implementers to use Freescale Semiconductor products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits or integrated circuits based on the information in this document.

Freescale Semiconductor reserves the right to make changes without further notice to any products herein. Freescale Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Freescale Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters which may be provided in Freescale Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Freescale Semiconductor does not convey any license under its patent rights nor the rights of others. Freescale Semiconductor products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Freescale Semiconductor product could create a situation where personal injury or death may occur. Should Buyer purchase or use Freescale Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold Freescale Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Freescale Semiconductor was negligent regarding the design or manufacture of the part.

Freescale™, the Freescale logo, and StarCore are trademarks of Freescale Semiconductor, Inc. All other product or service names are the property of their respective owners.

© Freescale Semiconductor, Inc. 2005, 2007.